

NAND-Schaltpläne mit dem Paket `relaycircuit` erstellen

```

1 begin{tikzpicture}
2   \draw (0,6.8) node [left] {\(+\)}
3     — (9,6.8);
4   \draw (0,0) node [left] {\(-\)}
5     — (9,0);
6   \draw (4.5,0) to[short,*-]
7     (4.5,0) node [ground] {};
8
9   \draw (7.4,2.5) to[short,*-]
10    (7.5,2.5) to[lamp] (9,2.5)
11    node[ground] {};
12
13  \draw (2.5,5.8) node[arbeits
14    relais] (a1) {};
15  \draw (2.5,4) node[arbeits relais]
16    (a2) {};
17  \draw (2.4,6.8) to[short,*-]
18    (a1.anschluss);
19  \draw (a1.ausgabe) —
20    (a2.anschluss);
21
22  \draw (2.5,1) node[ruhe relais]
23    (r1) {};
24  \draw (a2.ausgabe) —
25    (r1.anschluss);
26  \draw (r1.ausgabe) to[short,*-]
27    (2.4,0);
28  \draw (5,1) node[ruhe relais]
29    (r2) {};
30
31  \draw (r2.ausgabe) to[short,*-]
32    (4.9,0);
33  \draw (7.5,1) node[arbeits relais]
34    (a3) {};
35  \draw (7.5,4) node[ruhe relais]
36    (r3) {};
37  \draw (a3.anschluss) —
38    (r3.ausgabe);
39  \draw (a3.ausgabe) to[short,*-]
40    (7.4,0);
41  \draw (r3.anschluss) to[short,*-]
42    (7.4,6.8);
43
44  \draw (2.4,2.5) to[short,*-*]
45    (4.9,2.5) —| (a3.eingabe);
46  \draw (r2.anschluss) |-
47    (r3.eingabe);
48
49  \draw (0,4.7) node [left] {A}
50    to[short,*-] (0.2,4.7)
51    — (a2.eingabe);
52  \draw (0.2,4.7) |- (r1.eingabe);
53
54  \draw (0,2.1) node [left] {B}
55    to[short,*-] (0.4,2.1)
56    —| (r2.eingabe);
57  \draw (0.4,2.1) |- (a1.eingabe);
58 end{tikzpicture}

```

